




Asynchronous Design for Analogue Electronics

Alex Yakovlev



Motivation: A4A scope

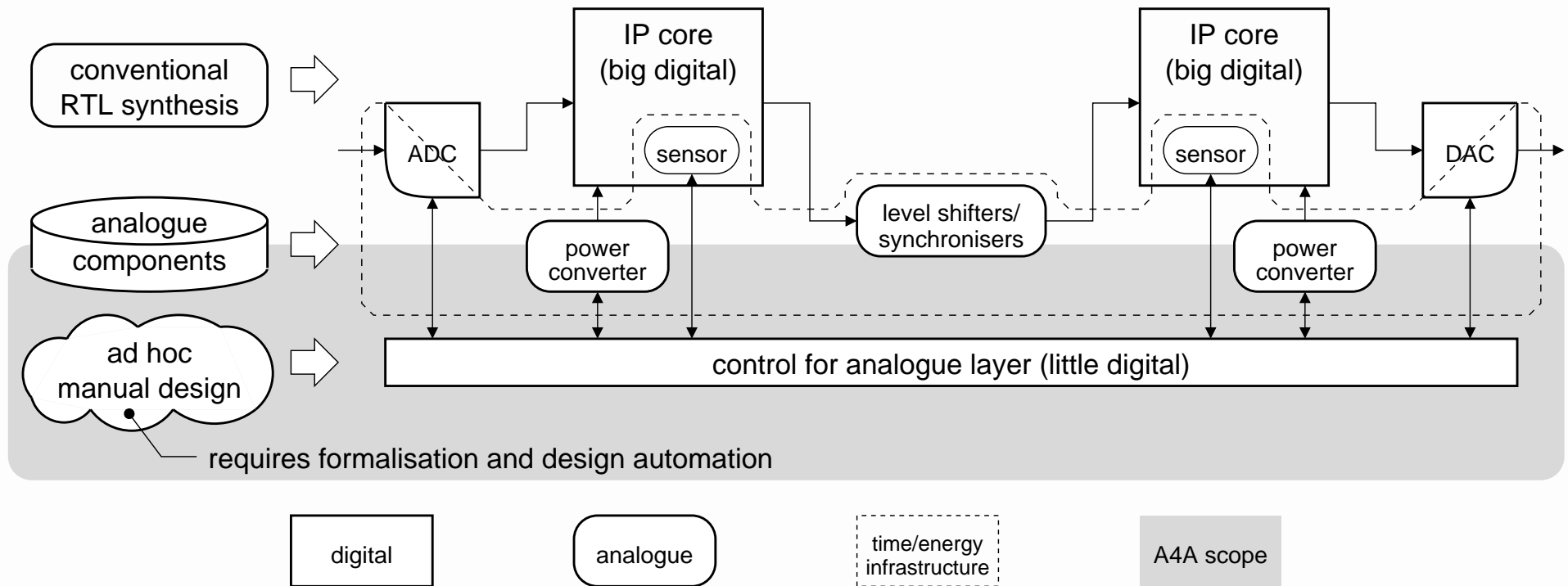


- Analogue and digital electronics are becoming more intertwined
- Analogue domain becomes more complex and itself needs digital control

Motivation: Power electronics context


- Efficient implementation of power converters is paramount
 - Extending the battery life of mobile gadgets
 - Reducing the energy bill for PCs and data centres (5% and 3% of global electricity production respectively)
- Need for responsive and reliable control circuitry - *little digital*
 - Millions of control decisions per second for years
 - An incorrect decision may permanently damage the circuit
- Poor EDA support
 - Synthesis is optimised for data processing - *big digital*
 - *Ad hoc* solutions are prone to errors and cannot be verified

Basic buck converter: Schematic

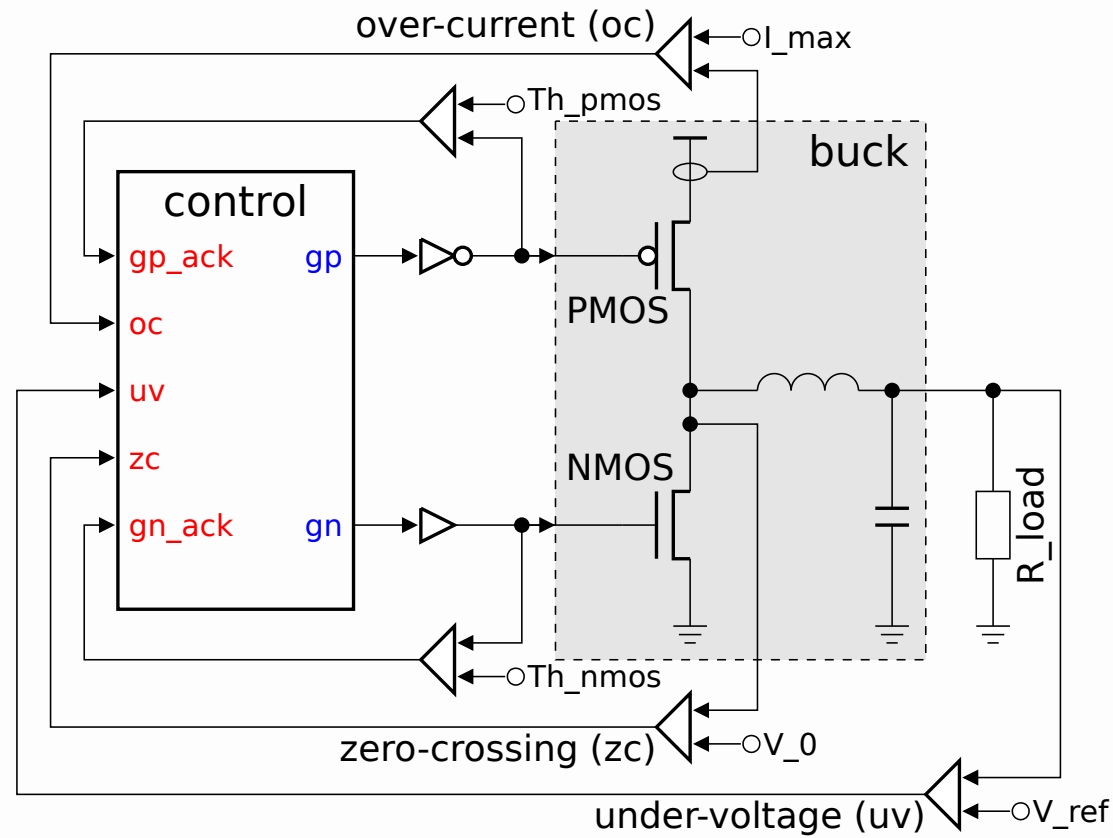


- In the textbook buck a diode is used instead of NMOS transistor

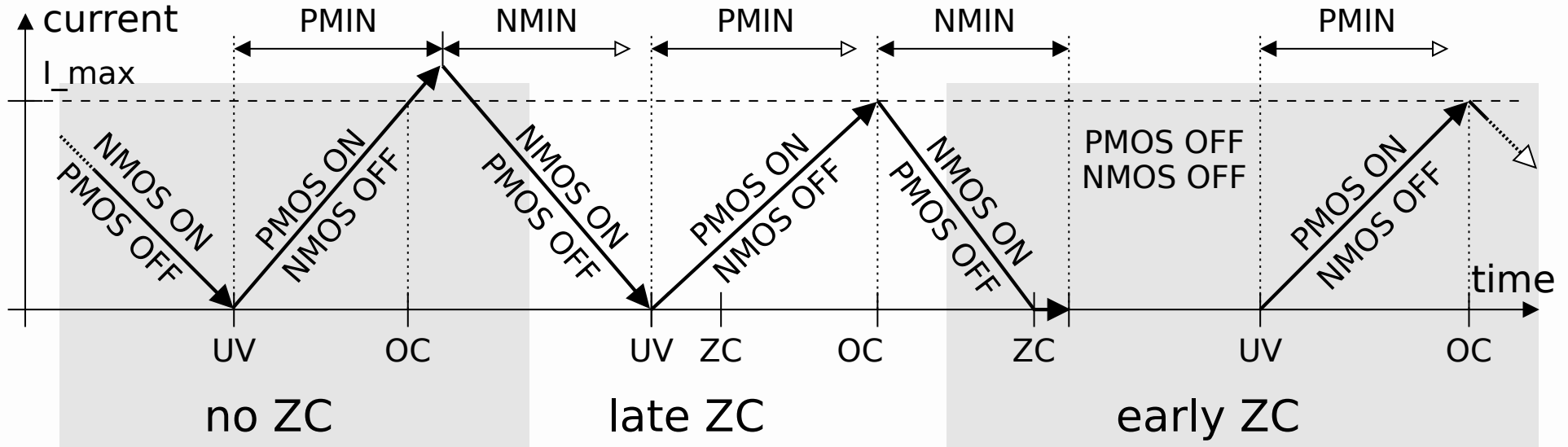Basic buck converter: Informal specification



- **no ZC** – under-voltage without zero-crossing
- **late ZC** – under-voltage before zero-crossing
- **early ZC** – under-voltage after zero-crossing

Multiphase buck converter: Schematic

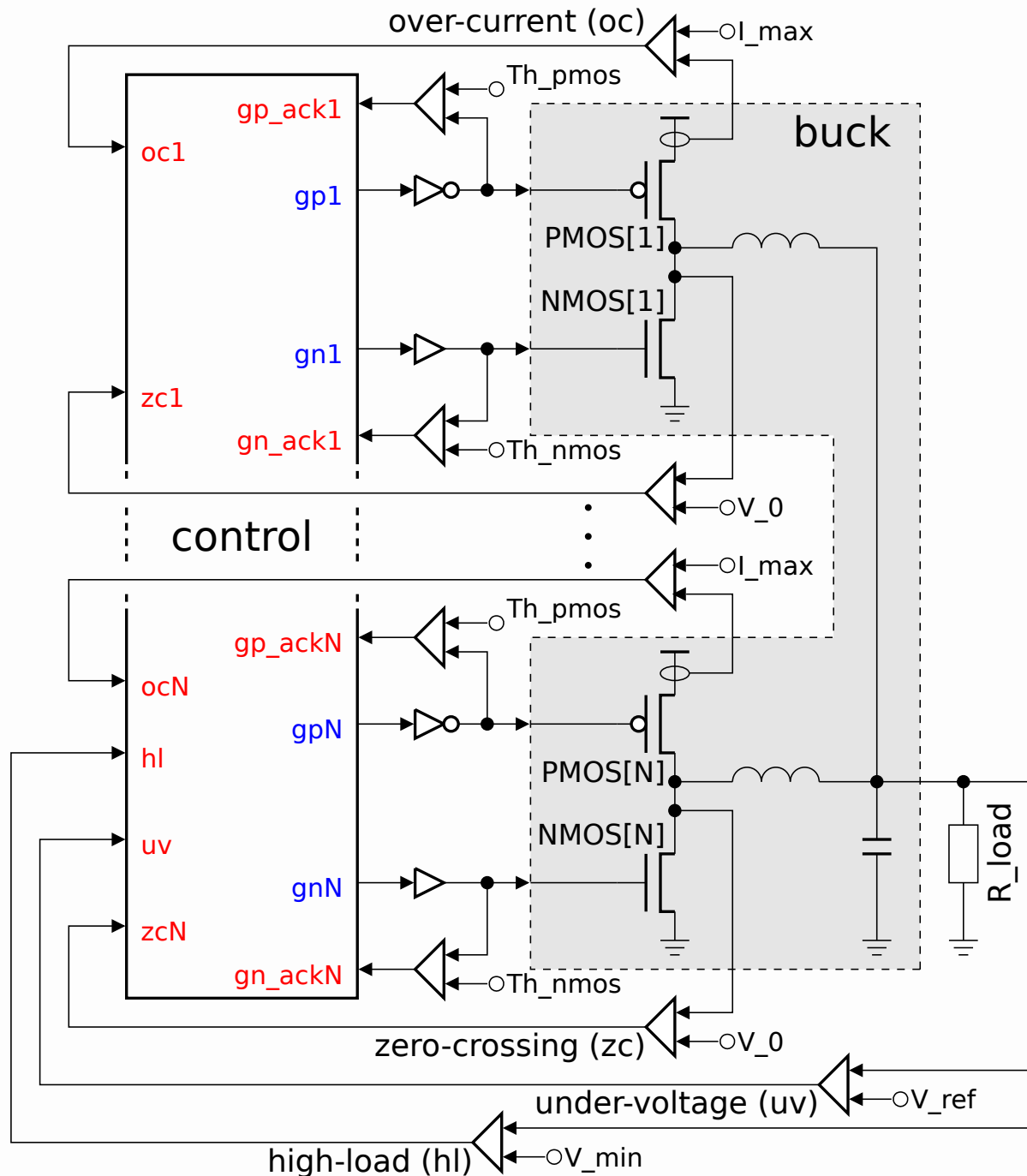

Multiphase buck converter: Informal specification

- Normal mode
 - Phases are activated sequentially
 - Phases may overlap
- High-load mode
 - All phases are activated simultaneously
- Benefits
 - Faster reaction to the power demand
 - Heat dissipation from a larger area
 - Decreased ripple of the output voltage
 - Smaller transistors and coils


Synchronous design

- Two clocks: phase activation ($\sim 5\text{MHz}$) and sampling ($\sim 100\text{MHz}$)
 - ☺ Easy to design (RTL synthesis flow)
 - ☹ Response time is of the order of clock period
 - ☹ Power consumed even when idle
 - ☹ Non-negligible probability of a synchronisation failure
- Manual ad hoc design to alleviate the disadvantages
 - ☹ Verification by exhaustive simulation

Asynchronous design


- Event-driven control decisions
 - ☺ Prompt response (a delay of few gates)
 - ☺ No dynamic power consumption when the buck is inactive
 - ☺ Other well known advantages
 - ☹ Insufficient methodology and tool support
- Our goals
 - Formal specification of power control behaviour
 - Reuse of existing synthesis methods
 - Formal verification of the obtained circuits
 - Demonstrate new advantages for power regulation (power efficiency, smaller coils, ripple and transient response)

High-level architecture: Token ring

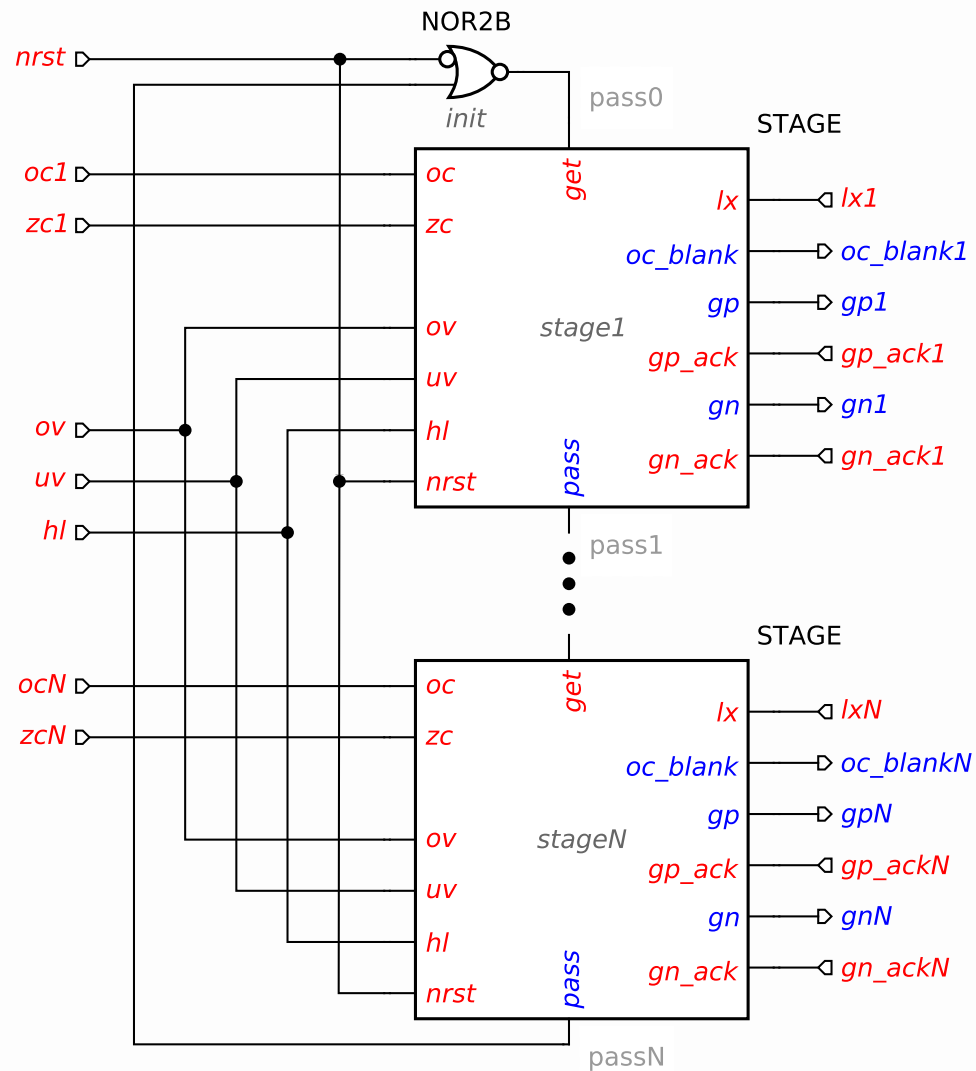

- No need for phase activation clock

High-level architecture: Charging stage

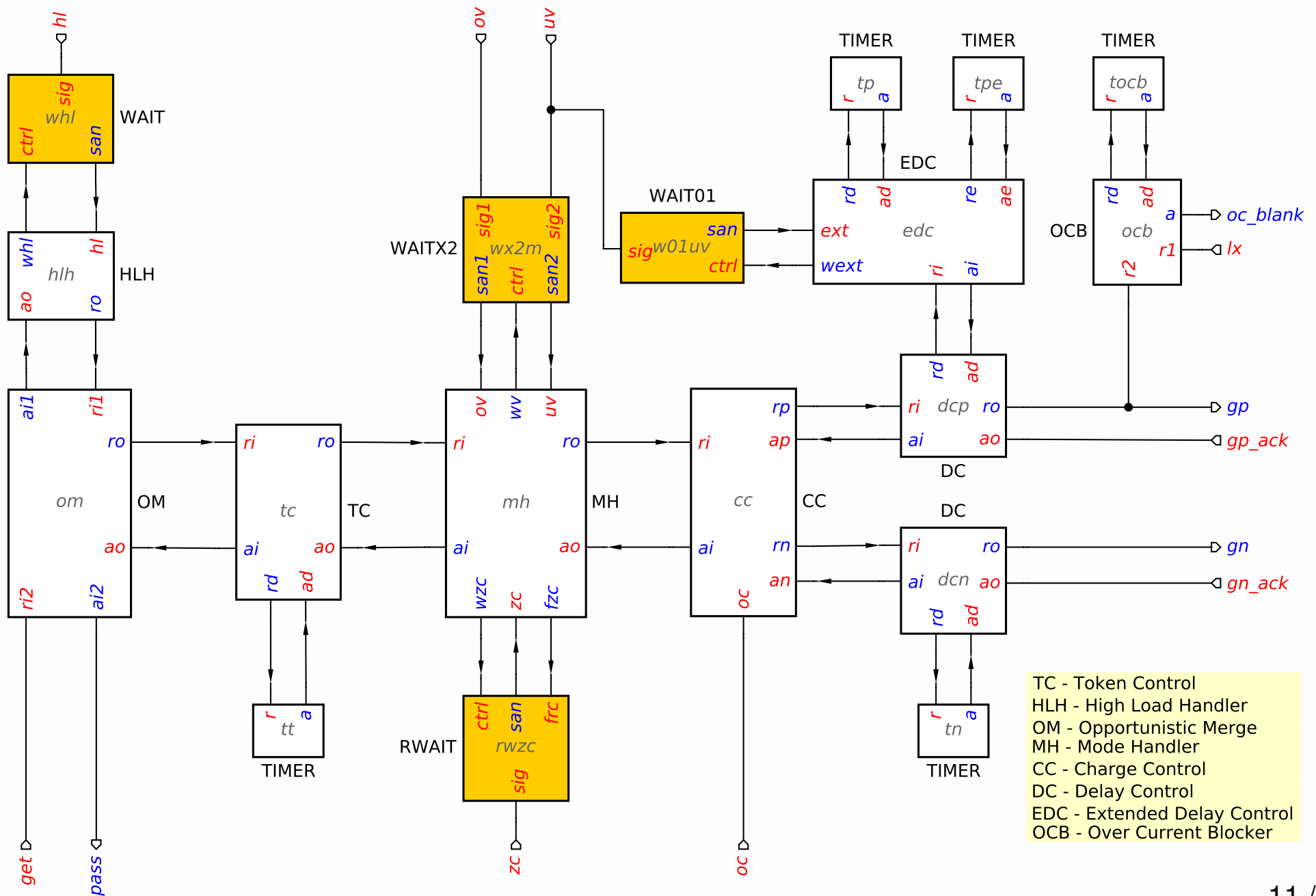


A2A components


- Interface analogue world of “dirty” signals
- Provide hazard-free “sanitised” digital signals for asynchronous control
- Library of A2A components
 - **WAIT / WAIT0** – wait for stable 1 / 0 on analogue input and latch it until explicit release signal
 - **RWAIT / RWAIT0** – WAIT element with a possibility to persistently cancel the waiting request
 - **WAIT01 / WAIT10** – wait for a rising / falling edge
 - **WAITX / WAITX2** – wait for one of analogue signals in a mutually exclusive way using 4-phase / 2-phase control signalling
 - **SAMPLE** – sample the state of analogue signal

A2A components: WAIT element


- STG specification

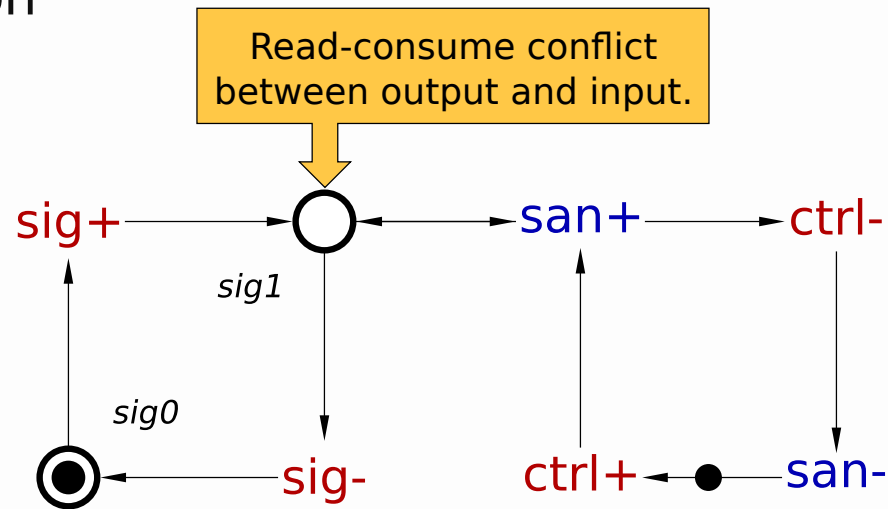

- ME-based solution

 

- Gate-level implementation

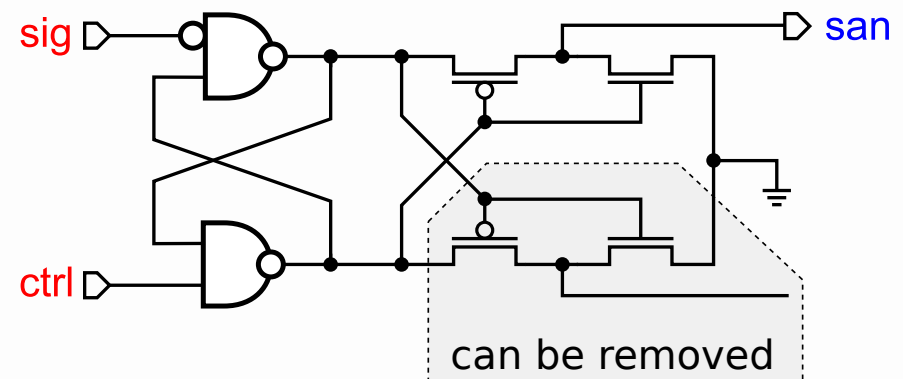

Synthesis flow

- Manual decomposition of the system into modules
 - To create formal specification from informal requirements (feedback loop with engineers)
 - To simplify specification and synthesis
 - Some modules are reusable
 - Some modules (A2A components, Opportunistic Merge) are potential standard components
- Each component is specified using STGs
- Automatic synthesis into speed-independent circuits (arbitrary gate delays and some forks must be isochronic)

Formal verification

- STG verification
 - All standard speed-independence properties (consistency, output-persistency, complete state coding)
 - PMOS and NMOS are never ON simultaneously (to prevent from short circuit)
 - Some timers are used in a mutually exclusive way and can be shared
- Circuit verification
 - Conforms to the environment
 - Deadlock-free and hazard-free under the given environment

Tool support: WORKCRAFT

- Framework for *interpreted graph models* (STGs, circuits, FSMs, dataflow structures, etc.)
 - Interoperability between models
 - Elaborated GUI
- Includes many backend tools
 - PETRIFY – STG and circuit synthesis, BDD-based
 - PUNF – STG unfold
 - MPSAT – unfolding-based verification and synthesis
 - PCOMP – parallel composition of STGs

Tool support: WORKCRAFT

The screenshot displays the Workcraft software interface with several panels:

- *circuit-ZCH-map [circuit]:** A logic circuit diagram with inputs *ri*, *ai*, and *zc*, and outputs *ro* and *ao*. It includes a flip-flop and several logic gates.
- stg-ZCH [STG]:** A state transition graph with nodes and transitions labeled with signals like *ri+*, *ro+*, *ao+*, *ai+*, *ro-*, *ao-*, *ai-*, *ri-*, *zc+*, and *zc-*. It highlights regions for "late or no ZC" and "early ZC".
- *circuit-ZCH-map 1 [STG]:** A detailed state transition graph showing the internal state elements *U1+*, *U1-*, *U4+*, and *U4-*.
- pcompressresult6863112684546701504 [STG]:** A complex state transition graph representing a compressed model.
- Property editor [model]:** Shows the environment path: `Environment... /stg-ZC...`
- Tool controls:** Includes icons for zooming, panning, and refreshing.
- Editor tools:** Includes icons for selection, text input, and navigation.
- Output:** Displays the following code:

```
INORDER = ao ri zc ai ro csc0;  
OUTORDER = [ai] [ro] [csc0];  
[ai] = csc0 ao'; # gate and2_1:combinational  
[1] = ri' zc' ro'; # gate nor3:combinational  
#PRAGMA: zero delay  
[2] = ao'; # gate inv:combinational  
[ro] = [1]' csc0' + [2]' ri'; # gate oai22:combinational  
[csc0] = csc0 [1]' + ao'; # gate sr_nor:async  
  
# Set/reset pins: reset(ro)  
Exporting model "Untitled" to file "/tmp/workcraft-circuit-ZCH-map-8245652389417126911/dev.g".
```
- Message:** A dialog box stating: "Under the given environment (stg-ZCH.work) the circuit is: * conformant * deadlock-free * hazard-free".
- workspace:** Shows the project structure:


```
workspace  
- workspace  
- External  
  - circuit-ZCH-map 1.work  
  - circuit-ZCH-map.work *  
  - stg-ZCH.work  
  - pcompressresult68631126845
```

Simulation results


- Verilog-A model of the 3-phase buck
- Control implemented in TSMC 90nm
- AMS simulation in CADENCE NC-VERILOG
- Synchronous design
 - Phase activation clock – 5 MHz
 - Clocked FSM-based control – 100 MHz
 - Sampling and synchronisation
- Asynchronous design
 - Phase activation - token ring with 200 ns timer (= 5 MHz)
 - Event-driven control (input-output mode)
 - Waiting rather than sampling (A2A components)

Simulation results

synchronous

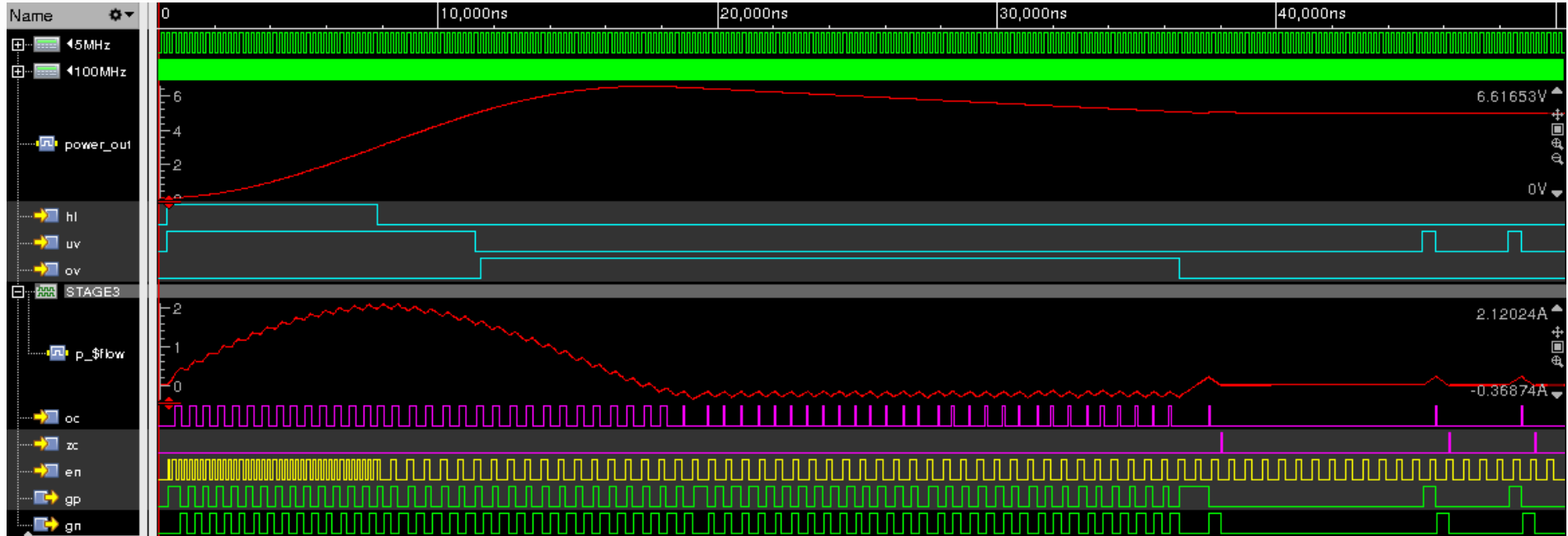

asynchronous

 


AMS Trends & Challenges

- Key drivers
 - Internet of Things
 - Mobile computing
 - Automotive electronics
- Trends
 - Technology scaling
 - Multiple power and time domains
 - Analog and digital integration
- Challenges
 - Tighter reliability margins
 - Concurrent analog and digital analysis
 - Short development cycle

What this means for AMS?



- Achieving better verification of **analog and digital blocks**
- Verifying the increasing amount of **digital logic in analog designs**
- Creating a **higher level of abstraction** for analog and mixed signal blocks
- **Automating** the manual custom design steps
- Adopting **circuit analytics** that tell **why** and **where** the circuit is failing to perform

Advanced AMS design flow


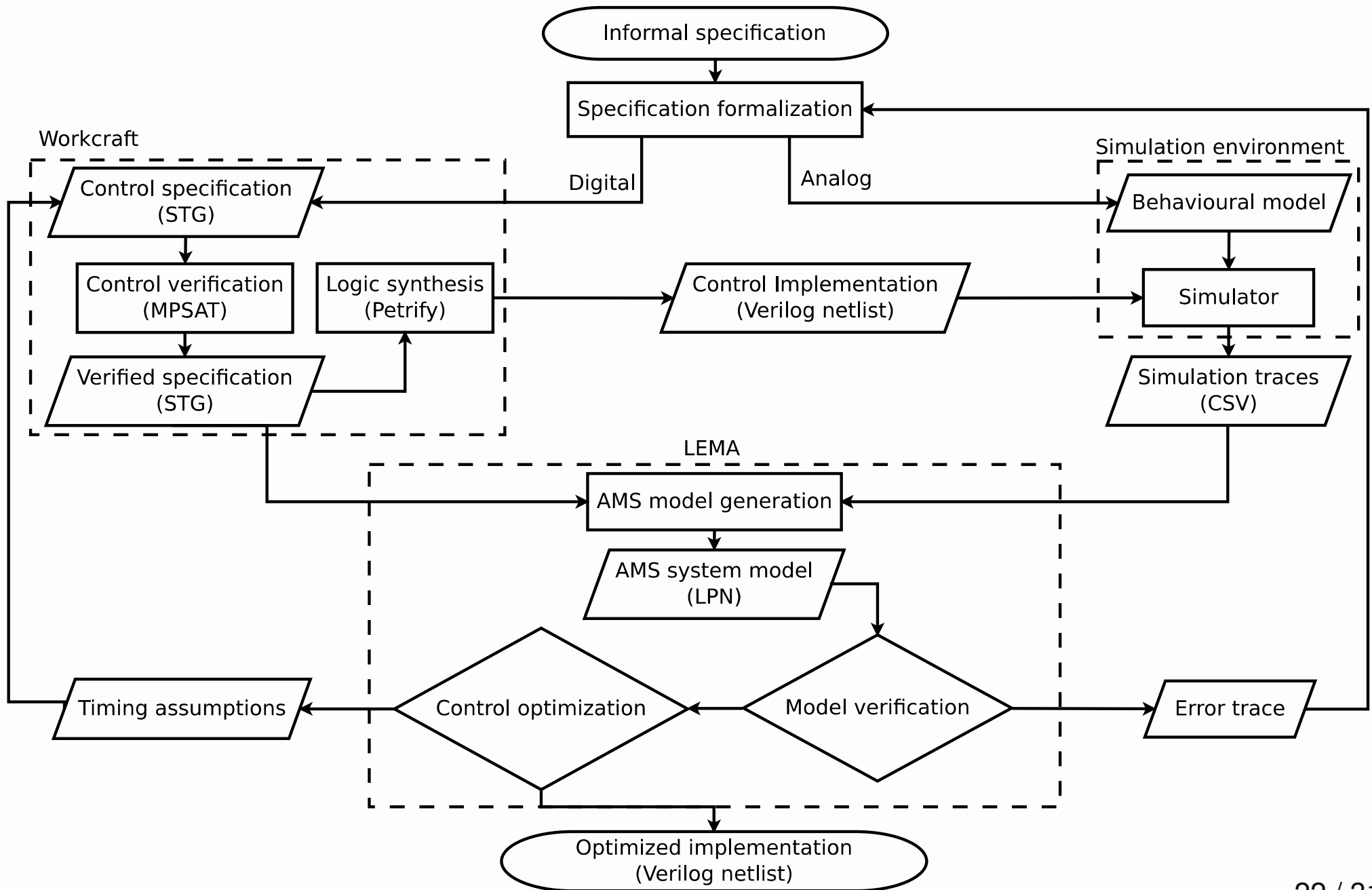


AMS flow: Tool support

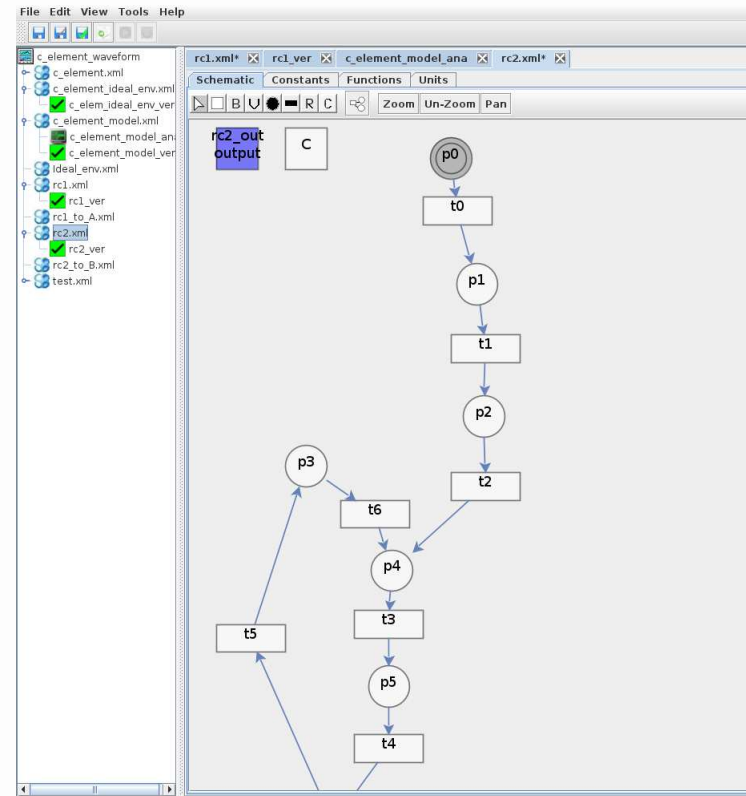
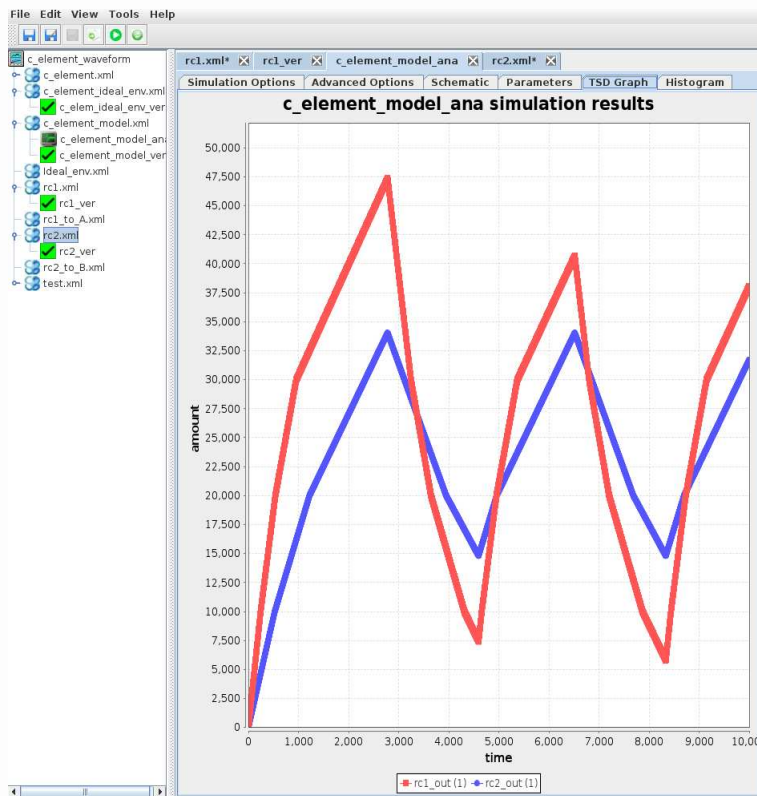
- WORKCRAFT – synthesis and verification of async. circuits
- LEMA – modelling and verification of AMS circuits
- Model generation from simulation traces
- Property expression and checking



AMS flow: Basic buck

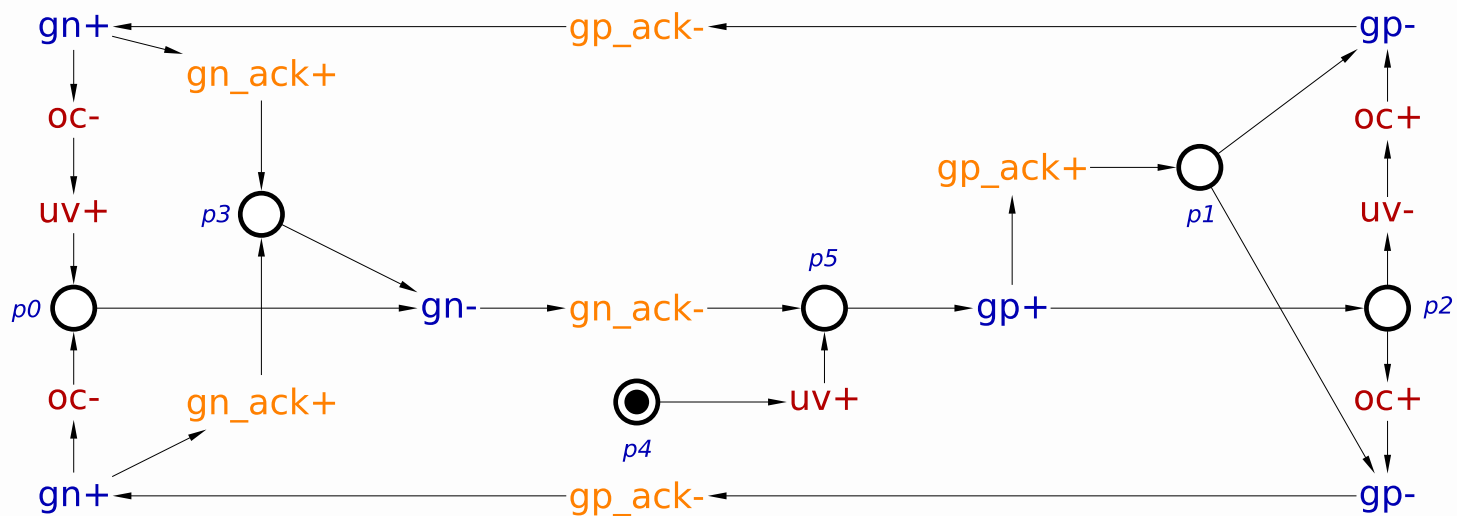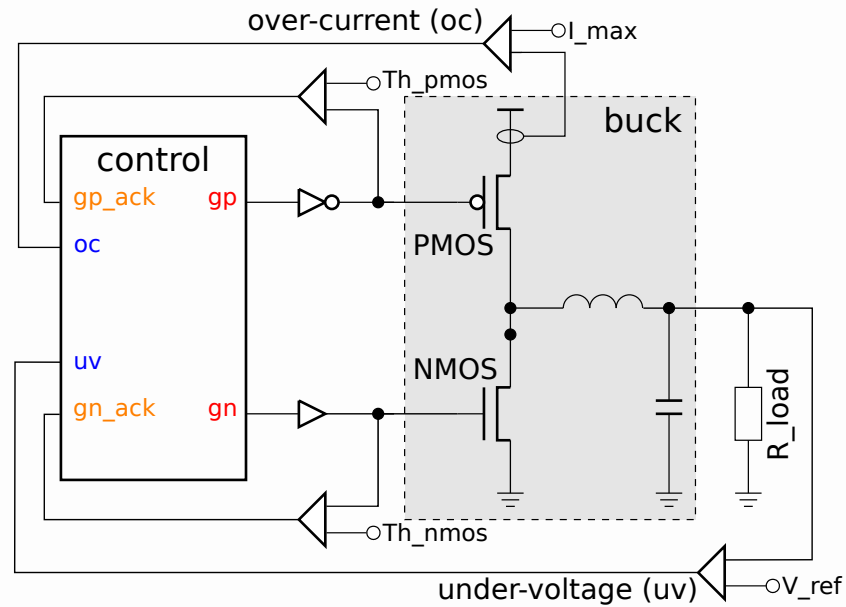


AMS flow: Model generation example

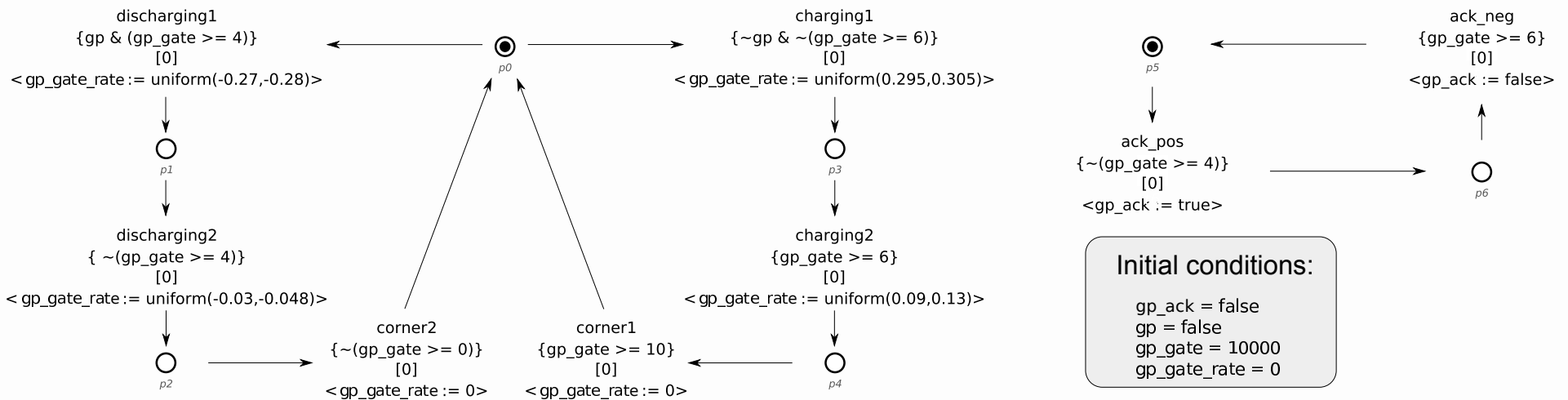 


AMS flow: Optimised specification

- Concurrency reduction

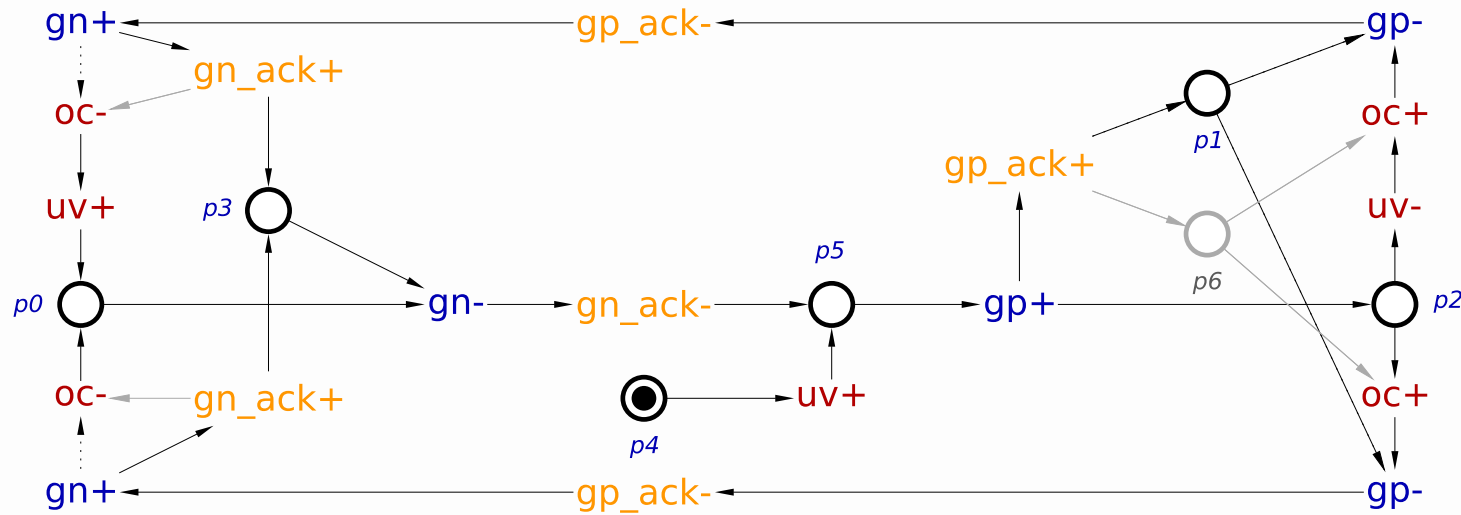


- Scenario elimination

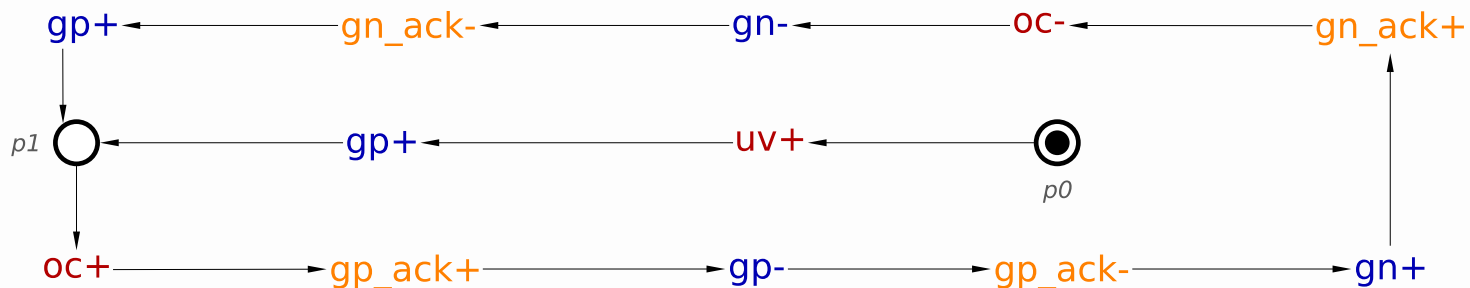


ADC: Sampling schemes



- Synchronous

 

- Asynchronous

 


ADC: Asynchronous design

 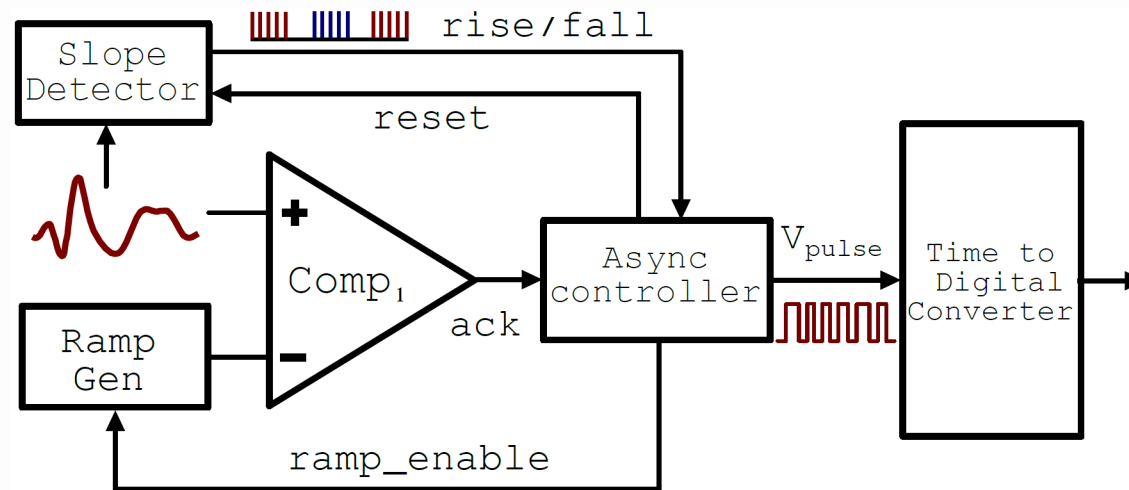


ADC: Specification and implementation

- STG specification

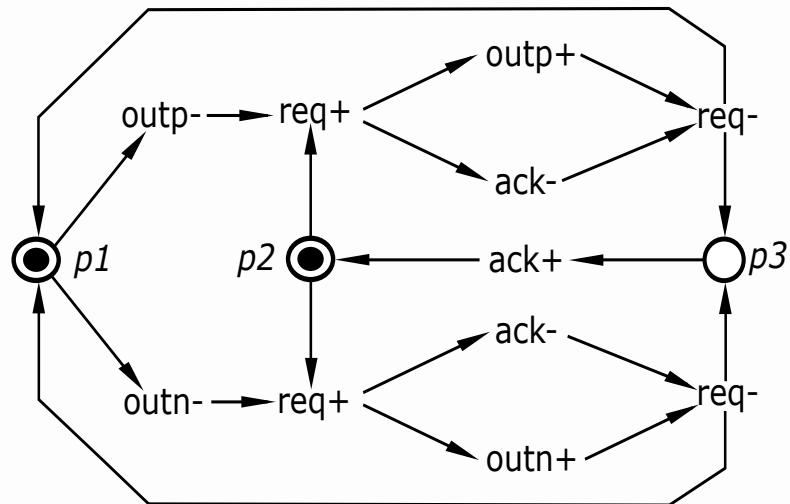

- Speed-independent implementation

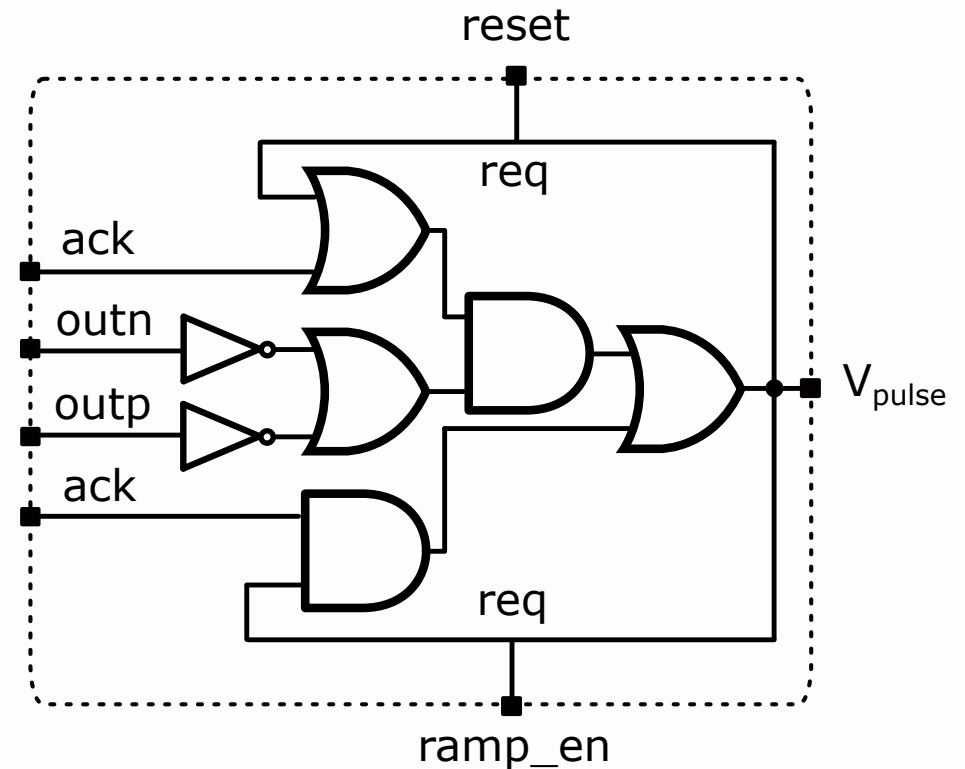

Conclusions

- Fully asynchronous design of multiphase buck controller
 - Quick response time: few gate delays, all mutexes are outside the critical path
 - Reliable: no synchronisation failures
- Design flow is automated to large extent
 - Automatic logic synthesis
 - Formal verification at the STG and circuit levels
 - Library of A2A components
- Vision for an advanced AMS design flow

Acknowledgements

- A4A team
 - Newcastle University: *Vladimir Dubikhin, Victor Khomenko, Andrey Mokhov, Danil Sokolov, Prof. Alex Yakovlev*
 - Dialog Semiconductor: *David Lloyd*
 - University of Utah: *Prof. Chris Myers*
- EPSRC for funding A4A project (EP/L025507/1)
- Design automation
 - WORKCRAFT – <http://workcraft.org/>
 - LEMA – <http://www.async.ece.utah.edu/LEMA>
- Recent publications
 - D. Lloyd, R. Illman: “*Scan insertion and ATPG for C-gate based asynchronous designs*”, SNUG- 2014.
 - D. Sokolov, et. al: “*Design and verification of speed-independent buck controller*”, ASYNC-2015.
 - V. Dubikhin, et. al: “*Design of mixed-signal systems with asynchronous control*”, IEEE Design & Test (to appear).